

FOCUSED REVIEW

Focused Review: Kirchhoff's Rules and Multiloop Circuits — Foundational

Review the essential ideas, relationships, and problem-solving tools for Kirchhoff's Rules and Multiloop Circuits.

 TIME 15–20 minutes	 BEST FOR Focused review	 FINISH WITH Greater confidence
---	--	---

After this focused review, you'll be able to...

recognize the key concepts, reinforce your problem-solving skills, and continue with greater confidence.

HOW TO USE THIS GUIDE

Work through the stages in order. Write directly in the spaces provided, check your work in the Solutions section, and finish by choosing the next resource that matches your confidence.

Choose how you want to review: work through this guide, follow the online review, or watch the video review.

Start the Review Online →

Watch the Video Review →

YOU WILL NEED

Pencil or pen • Calculator if needed • Approximately 15–20 minutes

FR-02 • COURSE ALIGNMENT

Course Alignment

This Physics Sensei Unit Review is an independent learning resource. Use it to reinforce key concepts, prepare for homework, or review before a quiz or exam.

RESOURCE: Physics Sensei Unit Review
UNIT ID: EME-U08
TOPIC: Kirchhoff's Rules and Multiloop Circuits
COURSE LEVEL: Foundational

BEST USED

- ✓ After learning the unit
- ✓ Before starting homework
- ✓ Before a quiz or exam

FR-03 • YOUR REVIEW PLAN

Your Review Plan

Complete these six focused stages in order. Each stage reinforces your understanding and prepares you for a final confidence check.

6 stages • Approximately 15–20 minutes

1 Warm-Up Check Refresh key ideas.	2 Core Concepts Reinforce the essentials.	3 Guided Practice Strengthen key skills.
4 Confidence Check Confirm your understanding.	5 Summary Remember the essentials.	6 Next Step Choose your next step.

PRINTING TIP

For student copies, print double-sided and keep the Solutions section after the student activities so learners attempt each activity before checking their work.

FR-04 • STAGE 1 OF 6

Warm-Up Check

Before you begin, take a minute to reactivate what you already know. This quick warm-up will help you focus on the most important ideas before moving on.

WARM-UP 1**Key Ideas**

What physical quantity is conserved at a circuit junction?

Explain your reasoning and record your response.

WARM-UP 2**Common Mistakes**

A calculated branch current is negative. What does its sign tell you?

Explain your reasoning and record your response.

FR-04 • WARM-UP CHECK CONTINUED

WARM-UP 3

Quick Application

A 12 V rise balances 5 V and 4 V drops. What is the remaining drop?

Explain your reasoning and record your response.

Ready to strengthen your understanding?

You've refreshed the most important ideas. Now reinforce the concepts you'll use most often.

Continue to Core Concepts →

FR-05 • STAGE 2 OF 6

Core Concepts

Let's reinforce the most important concepts you'll need to solve problems with confidence. Focus on the ideas that appear most often in homework, quizzes, and exams.

KEY CONCEPT 1

Junction rule

Charge conservation requires the total current entering a junction to equal the total leaving it.

$$\sum I_{in} = \sum I_{out}$$

EXAMPLE If 3 A enters and 1 A leaves along one wire, the other outgoing current is 2 A.

SENSEI NOTE Choose reference arrows before assigning current signs.

KEY CONCEPT 2

Loop rule

Energy conservation requires the sum of voltage rises and drops around a closed steady-state loop to be zero.

$$\sum \Delta V = 0$$

EXAMPLE A 12 V rise balances drops of 4 V, 5 V, and 3 V.

SENSEI NOTE A resistor is a drop when traversed in the assumed current direction.

Ready to apply these ideas?

You've reinforced the essential concepts. Now strengthen your problem-solving skills by working through a few guided examples.

[Continue to Guided Practice →](#)

FR-06 • STAGE 3 OF 6

Guided Practice

Now apply the key concepts you've just reviewed. Work through these focused practice activities to reinforce your problem-solving skills before the final confidence check.

PRACTICE 1**Guided Example**

At a junction 3 A enters and 1 A leaves. Find the other outgoing current.

Show the circuit equations, substitutions, and result.

PRACTICE 2**Independent Check**

In a closed loop, a 12 V source opposes 4 V and 5 V drops. Find the third voltage drop.

Show the circuit equations, substitutions, and result.

Ready for a confidence check?

You've reinforced the essential skills through focused practice. Now confirm your understanding with two short questions.

Continue to Confidence Check →

FR-07 • STAGE 4 OF 6

Confidence Check

You've reinforced the key concepts and practiced the essential skills. Now confirm you're ready to move forward by completing these short confidence checks.

CONFIDENCE CHECK 1

Check your understanding

If a calculated current is negative, what does that mean?

Write your answer before consulting the solutions.

CONFIDENCE CHECK 2

Check your understanding

Why must the net potential change around a closed steady-state loop vanish?

Write your answer before consulting the solutions.

HOW DID IT GO?

I answered ____ of 2 questions correctly.

Use the Solutions section to check your reasoning, then take one final look at the essential ideas.

You've confirmed your understanding.

Take one final look at the essential ideas before choosing your next step.

Continue to Summary →

FR-08 • STAGE 5 OF 6

Summary

Before moving on, take one final look at the essential ideas you'll want to remember.

KEY TAKEAWAY 1**Junction rule**

Charge conservation requires the total current entering a junction to equal the total leaving it.

KEY TAKEAWAY 2**Loop rule**

Energy conservation requires the sum of voltage rises and drops around a closed steady-state loop to be zero.

MY ONE-SENTENCE SUMMARY

In my own words, the most important idea is:

Ready for your next step?

You've reviewed the essential ideas one last time. Now choose the resource that best matches how confident you feel.

Continue to Next Step →

ANSWER KEY • CHECK AFTER ATTEMPTING

Solutions and Explanations

Use these solutions to check your reasoning—not only your final answer. Replace each placeholder with a concise answer and the essential explanation.

WARM-UP • ACTIVITY 1

Key Ideas

Electric charge.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

WARM-UP • ACTIVITY 2

Common Mistakes

The actual current is opposite the assumed arrow.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

WARM-UP • ACTIVITY 3

Quick Application

3 V.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

SOLUTIONS • GUIDED PRACTICE

PRACTICE 1**Guided Example**

2 A leaves.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

PRACTICE 2**Independent Check**

$12 - 4 - 5 - V = 0$, so $V = 3 \text{ V}$.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

SOLUTIONS • CONFIDENCE CHECK**CONFIDENCE CHECK 1**

The current flows opposite to the assumed direction.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

CONFIDENCE CHECK 2

A charge returns to its starting potential energy; the signed rises and drops balance.

WHY IT WORKS This result follows from charge or energy conservation with a consistent sign convention.

READINESS GUIDE

2 correct: You're ready to continue. • 1 correct: Review the missed idea, then continue. • 0 correct: Revisit Core Concepts or choose more practice.

FR-09 • STAGE 6 OF 6

Next Step: Continue Learning

Great work! You've completed this focused review. Choose the next resource that best matches how confident you feel.

? I'm Still Unsure Review the focused review again to strengthen the essential concepts. Review Again →	⊙ I Need More Practice Build confidence with additional practice problems. Go to Practice →	✓ I'm Ready Continue to the next topic or learning resource. Continue →
---	---	---

RECOMMENDED LINKS

Review this topic again →

Find additional practice →

Choose another type of physics help →

Continue reviewing with these companion resources.

Start the Review Online →

Watch the Video Review →

TEMPLATE-ONLY PRODUCTION FIELDS — DELETE BEFORE EXPORTING

PHYSICS HELP THAT MAKES SENSE

A Physics Sensei review never ends at the last question. It always guides you toward the next useful step.

PhysicsSensei.com